
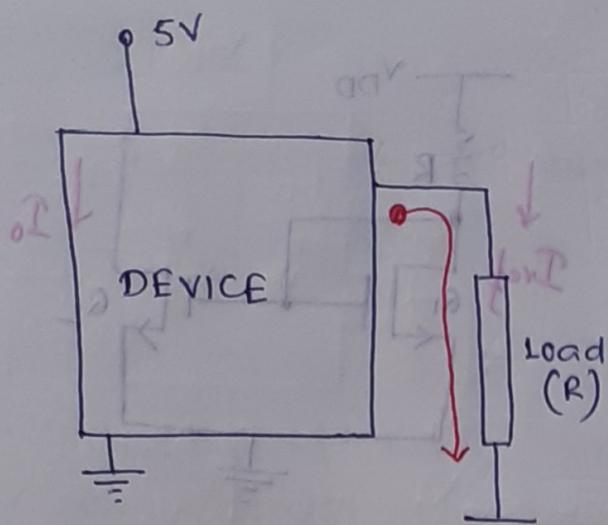


*> Current source & sink →

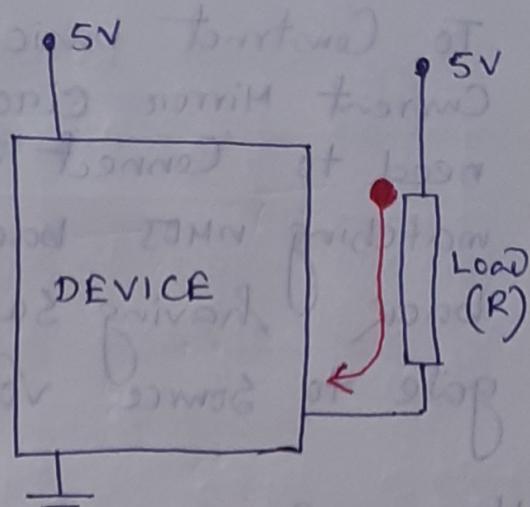

<Current Source>

[Current flow out of device]



<Current Sink>

[Current flow into device]

Example :- A series resistor and LED connected between microcontroller pin and ground. When microcontroller pin becomes active high, the microcontroller will source current to the load & LED glows.

Example :- Current flow from power supply through the load & into the device.


*> A Current Sink/Source is a two terminal component whose current at any instant of time is independent of the voltage across it.

{ A simple Current Source → pMOS
A simple Current Sink → nMOS }

*> To act as a Current Sink/Source, MOS should be operated in saturation region; Because here current is constant irrespective of V_{DS} for the given V_{GS} [V_{DS,min} = V_{GS} - V_{TH}] to put in saturation.

* MOSFET Current Mirror :-

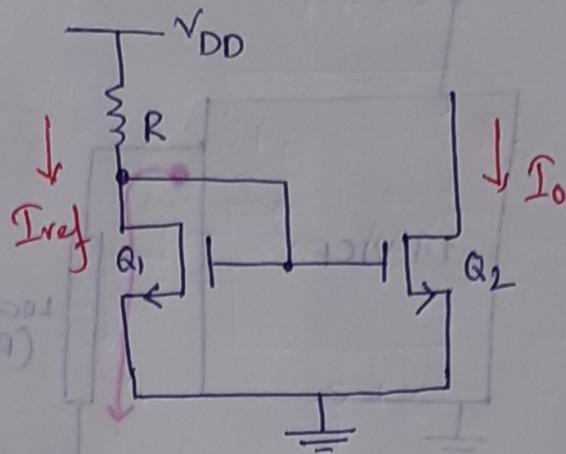To Construct basic Current Mirror circuit, need to Connect two matching nMOS back to back having same gate to source voltage.



Here, for Q_1 nMOS gate & drain are shorted. for both Q_1 and Q_2 V_{GS} are equal. ($V_{GSI} = V_{GS2}$). We know that, Condition for Saturation is,

$$V_{DS} \geq V_{GS} - V_{TH}$$

Now, for Q_1 , drain & gate terminal are shorted

so, $\left\{ \begin{array}{l} V_{DS} \geq V_{DS} - V_{TH} \\ \text{&} V_{GS} \geq V_{GS} - V_{TH} \end{array} \right. \} \quad \text{both conditions fulfilled}$

It means Q_1 operated in saturation region.

Now, $I_0 = \frac{1}{2} K_n_2 \cdot \left(\frac{W}{L}\right)_2 \left(V_{GS_2} - V_{TH_2}\right)^2$

and, $I_{ref} = \frac{1}{2} K_n_1 \cdot \left(\frac{W}{L}\right)_1 \left(V_{GS_1} - V_{TH_1}\right)^2$

As both the transistors are identical

$$\frac{I_0}{I_{ref}} = \frac{0.5 K_n_2 \left(\frac{W}{L}\right)_2 \left(V_{GS_2} - V_{TH_2}\right)^2}{0.5 K_n_1 \left(\frac{W}{L}\right)_1 \left(V_{GS_1} - V_{TH_1}\right)^2} = \frac{\left(\frac{W}{L}\right)_2}{\left(\frac{W}{L}\right)_1}$$

[So, when $\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_2 \rightarrow$ act as Current mirror.]

$$I_o = I_{ref}$$

acts as current mirror

Applications →

- i) Used as biasing element for superior O/P performance
< due to the variation in power supply, temperature >
- ii) used as active load element for amplifier stages;
which result high voltage gain at lower supply voltage; because of high output impedance of current mirror.

$$\left\{ \begin{array}{l} \text{Output impedance} \\ = \frac{\Delta V_o}{\Delta I_o} \\ = \infty \end{array} \right. \quad \left. \begin{array}{l} \text{in Saturation} \\ \Delta I_o \rightarrow 0 \end{array} \right.$$

** Small signal model vs Large signal model :-

The small signal model accounts for the behavior which is linear around an operating point.


When the signal is large in amplitude (more than $V_{cc}/5$, a rule of thumb); the behavior becomes non-linear.

* Differential amplifier (using MOSFET) :- DIBO

Here Common Resistance $\rightarrow R_s$.

$$V_o = A(V_1 - V_2)$$

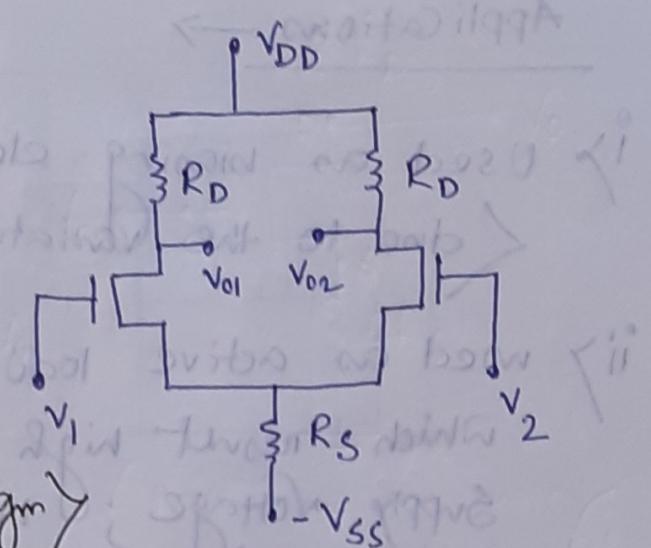mainly used to amplify the difference of two input signals.



DC Analysis :- < To determine g_m

We know that,

$$\text{i)} g_m = 2 \sqrt{K_n \cdot I_D} \quad \dots \textcircled{I}$$

$$\text{ii)} I_D = K_n \cdot (V_{GS} - V_{TH})^2 \quad \dots \textcircled{II}$$


In eqn. \textcircled{II} , I_D & V_{GS} are two unknown quantity.

To solve it, it required atleast two eqn. having V_{GS} & I_D .

< need to break the ckt in two half >

$$2R_s \left\{ \begin{array}{c} | \\ \square \\ | \end{array} \right\} 2R_s \Rightarrow \frac{2R_s \times 2R_s}{4R_s}$$
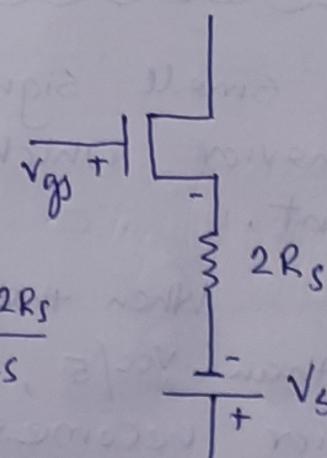
$$\therefore -V_{GS} - I_D \times 2R_s + V_{SS} = 0 \quad \textcircled{III}$$




Here value of V_{SS} & R_s given to the question. So using eqn. \textcircled{II} & \textcircled{III} , we can evaluate the value of I_D & V_{GS} .

Then using eqn. \textcircled{I} → easily find the value of g_m .

$$\begin{aligned} I_D &= K_n \cdot (V_{GS} - V_{TH})^2 \\ \frac{\partial I_D}{\partial V_{GS}} &= K_n \cdot 2(V_{GS} - V_{TH}) \\ &= K_n \cdot 2 \times \sqrt{\frac{I_D}{K_n}} \\ &= 2 \sqrt{K_n \cdot I_D} \end{aligned}$$

AC analysis < To find A_d >

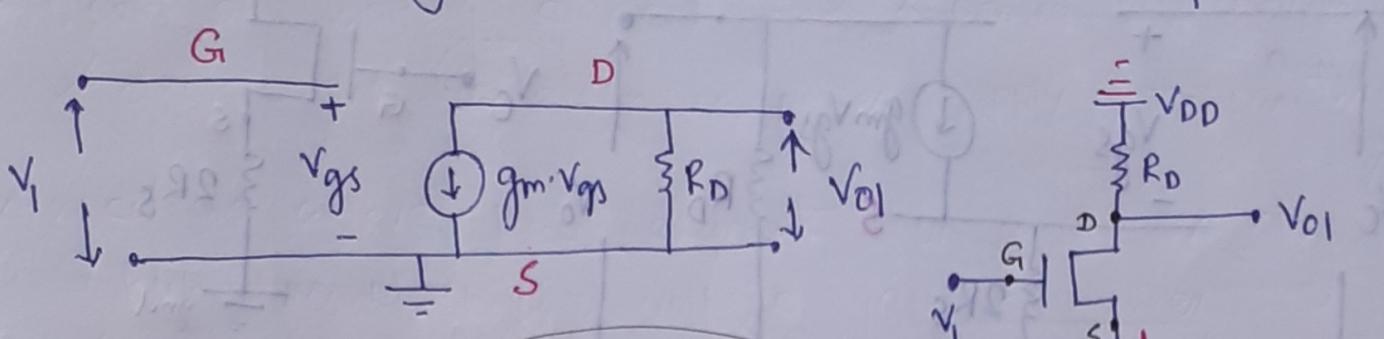for AC analysis, all the biasing DC voltage source need to be grounded. R_s become shorted.



$$\text{here, } V_{01} = (-g_m \times v_{gs}) \times R_D$$

$$\text{Similarly, } V_{02} = (-g_m \times v_{gs}) \times R_D$$

As the current flowing in opposite direction.

$$\text{for MOSFET 1} \rightarrow v_{gs} = \frac{V_d}{2}; V_{01} = -g_m \times \frac{V_d}{2} \times R_D$$

$$\text{for MOSFET 2} \rightarrow v_{gs} = -\frac{V_d}{2}; V_{02} = g_m \times \frac{V_d}{2} \times R_D$$

$$\therefore V_o = V_{02} - V_{01} = \frac{V_d}{2} \times g_m \times 2R_D = V_d \times g_m \times R_D$$

$$A_d = \frac{V_o}{V_d} = g_m \times R_D$$

{ differential mode gain }


N.B \Rightarrow $A_d = \text{differential mode gain}$.

Here, the amount of current flowing through the drain terminal (I_D) = $g_m v_{gs}$

$$\left\{ \begin{array}{l} g_m \cdot v_{gs} \\ = \frac{I_{ds}}{v_{gs}} \cdot v_{gs} \\ = I_{ds} \end{array} \right.$$

$$\left(\frac{29 \times mP}{29 \times mP + 1} \right) = \left| \frac{\frac{19 \times mP}{29 \times mP}}{\frac{19 \times mP}{29 \times mP + 1}} \right| = \left| \frac{19}{29} \right| = 99 \text{MS}$$

find Common mode gain (A_c) :-

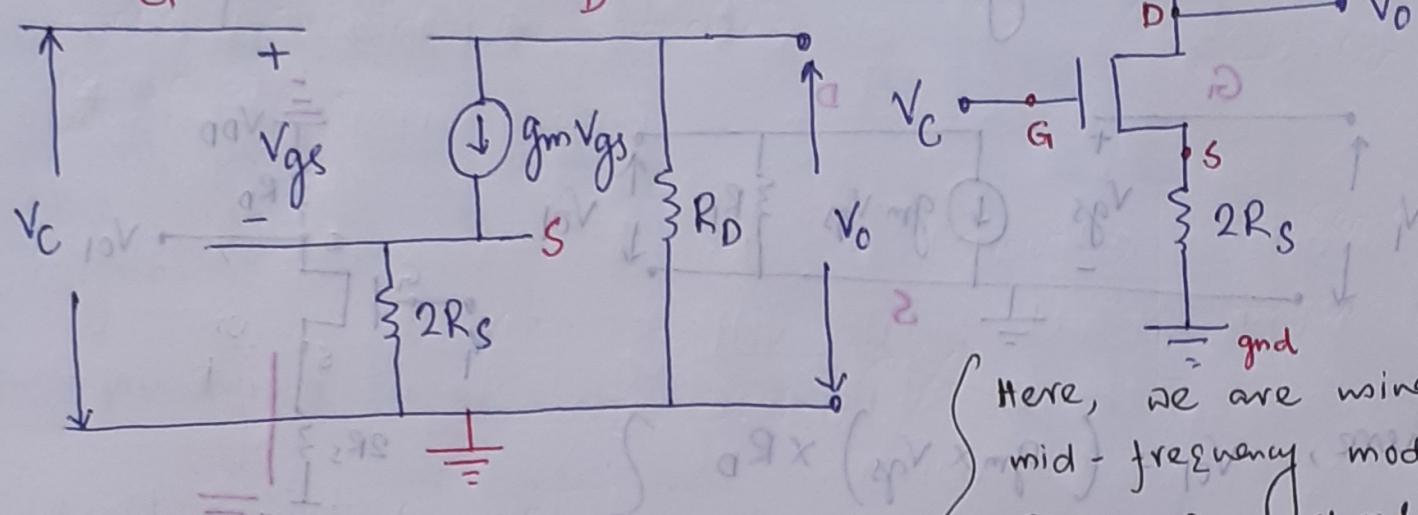

We know that,

$$A_c = \frac{V_o}{V_c}$$

Here, we are using mid-frequency model, where R_s should present in the CKT.

$$\text{here } V_o = (-g_m \times V_{gs}) \times R_D$$

$$\text{we know that, } V_{gs} = V_g - V_s \quad \left\{ \text{here } V_g = V_c \right\}$$

$$\text{and, } V_s = (g_m \times V_{gs}) \times 2R_s$$

$$\therefore V_{gs} = V_c - (g_m \times V_{gs}) \times 2R_s$$

$$\Rightarrow V_c = V_{gs} + (g_m \times V_{gs}) \times 2R_s = V_{gs} \left(1 + g_m \times 2R_s \right)$$

$$\therefore A_c = \frac{V_o}{V_c} = \frac{-g_m \times V_{gs} \times R_D}{V_{gs} \left(1 + g_m \times 2R_s \right)}$$

$$\therefore CMRR = \left| \frac{A_d}{A_c} \right| = \left| \frac{\frac{g_m \times R_D}{g_m \times R_D}}{\frac{1 + g_m \times 2R_s}{1 + g_m \times 2R_s}} \right| = \boxed{1 + g_m \times 2R_s}$$

$\underline{A_{cm}}$